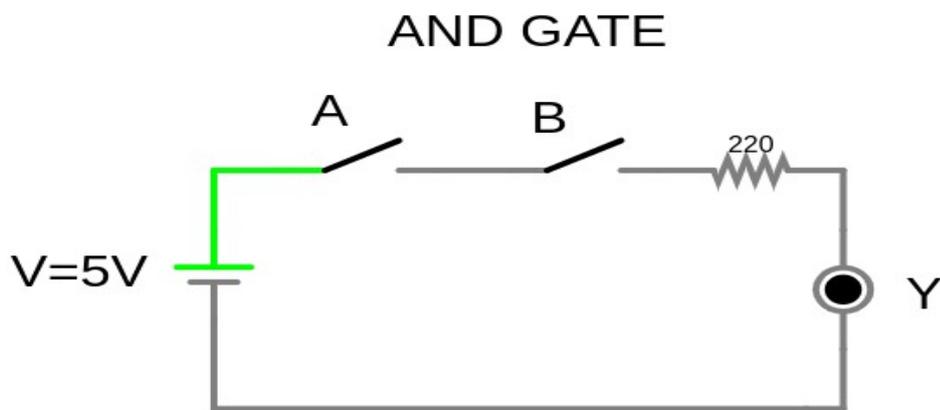


CircuitJS
AND Gate – Assignment

Assignment 1:

1. Using the **switches** and **LED** circuit, verify the **AND** gate truth table

AND gate with switches and LED



AND Gate Truth Table

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

Assignment 2:

1. With the **AND** gate component, check and verify the **AND** gate truth table

AND Gate component:

