 


CircuitJS
NOR Gate – Assignment

Assignment 1:

1. Connect the logic input and logic output to the **NOR** gate.
2. Use **Add Logic Input** and **Add Logic Output** to connect input and output of the **NOR** gate.
3. Label the input pins as **A** and **B** and output pin as **Y**.
4. Follow the truth table input values and verify the **NOR** Gate.

2- INPUT NOR Gate



Truth Table NOR Gate


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

Assignment 2:

Do this assignment with 3-input gate:

- Build a 3-input **NOR** gate as shown in the image.
- Label the input pins as A, B and C and the output pin as Y.
- Verify the truth table for the 3-input **NOR** gate.

3-INPUT NOR Gate

 

3-INPUT NOR Gate

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0